

215A Diagnostic Test Solutions

$$\textcircled{1} \quad \frac{V_{out}}{V_{in}} = -g_m R_L$$

$$\textcircled{2} \quad \frac{V_{out}}{V_{in}} = \frac{(1+g_m r_\pi) R_E}{r_\pi + (1+g_m r_\pi) R_E}$$

$$\textcircled{3} \quad \frac{(1+g_m r_\pi) R_E}{r_\pi + (1+g_m r_\pi) R_E} V_{in} \xrightarrow[-]{\quad} \frac{r_\pi R_E}{r_\pi + (1+g_m r_\pi) R_E}$$

$$\textcircled{4} \quad \left(\frac{1}{r_\pi} + g_m \right) V_{in} \xrightarrow[-]{\quad} \frac{r_\pi R_E}{r_\pi + (1+g_m r_\pi) R_E}$$

$$\textcircled{5} \quad I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \quad \text{If } V_{TH} \uparrow; I_D \downarrow.$$


\textcircled{6} At low V_{DS} , the transistor is in the triode region. In this plot, the device is in the deep triode region because I_D is a linear function of V_D :

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$


$$\approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) V_{DS}$$

$$\Rightarrow \frac{V_{DS}}{I_D} = R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$

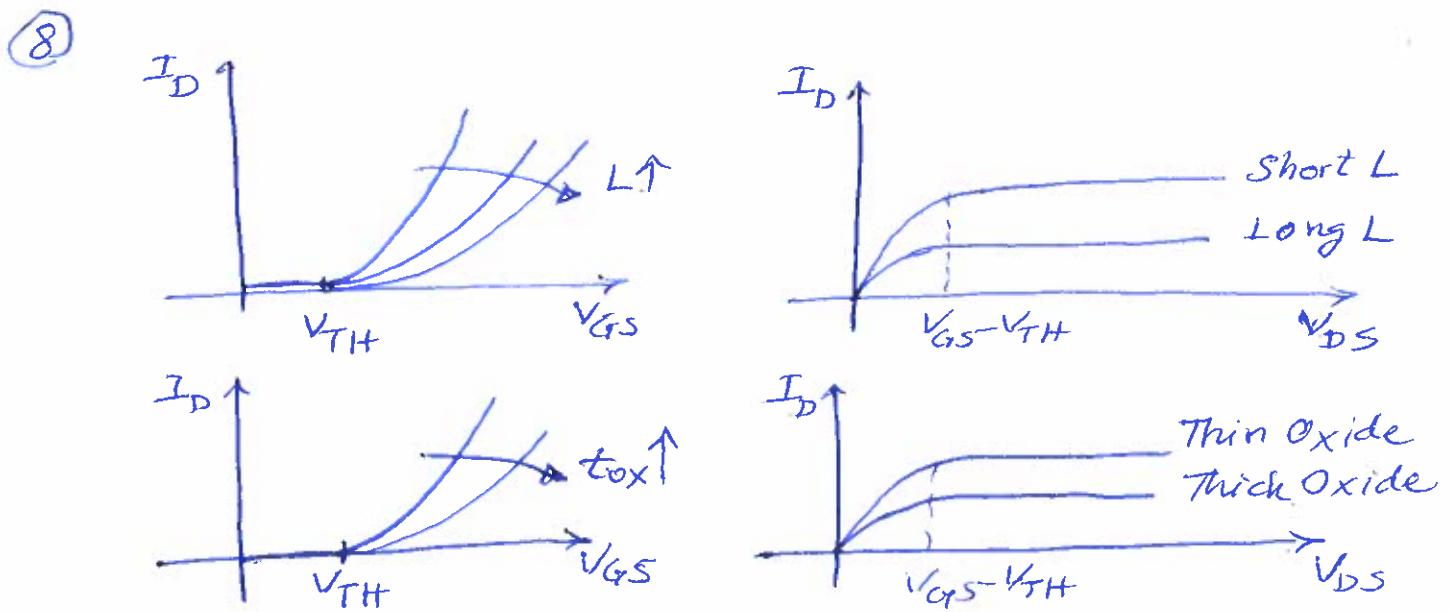\textcircled{7} The device turns on in saturation because V_{GS} begins to cross V_{TH} and hence $V_{GS} - V_{TH}$ is small. That is,
 $V_{DS} > V_{GS} - V_{TH}$.



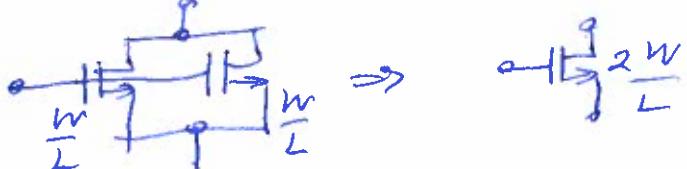⑨ Yes, the two can be lumped into one with twice the width:



⑩ $\lambda=0$ because I_D is independent of V_{DS} in the saturation region.

⑪ We guess that M₁ is in saturation and check at the end -

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (1V - 0.4V)^2 = 200 \mu A$$

$$V_{DS} = V_{DD} - R_D I_D = 0.8V \Rightarrow \text{saturated.}$$

If V_{GS} changes by 10 mV, the drain current changes by $g_m \times (10 \text{ mV}) = \mu_n C_{ox} \frac{W}{L} (1V - 0.4V) \times (10 \text{ mV}) = 8.7 \mu A$, yielding an output voltage change of $g_m \times (10 \text{ mV}) \times R_D = 33 \text{ mV}$.

⑫ At the edge, $V_{DS} = V_{GS} - V_{TH} = 0.6V \Rightarrow V_{DD} - R_D I_D = 0.6V$

$$\Rightarrow I_D = 0.24 \text{ mA} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0.6V)^2 \Rightarrow \frac{W}{L} = 13.3$$


⑬ $V_{GS} = V_{DD} - I_D R_D + V_{TH} = V_{DD} + V_{TH} - \frac{R_D}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$
 $\Rightarrow V_{GS}$ can be found from the quadratic.

⑭ $g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \Rightarrow g_m \text{ doubles. } I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \Rightarrow V_{GS} - V_{TH} \text{ const.}$

⑮ $r_o \approx \frac{1}{\lambda I_D} = 10 \text{ k}\Omega$, $\Delta I_D = \frac{4V_{DS}}{r_o} \approx 50 \mu\text{A}$

⑯ If L is doubled, λ is halved $\Rightarrow r_o \approx 20 \text{ k}\Omega \Rightarrow \Delta I_D \approx 25 \mu\text{A}$.

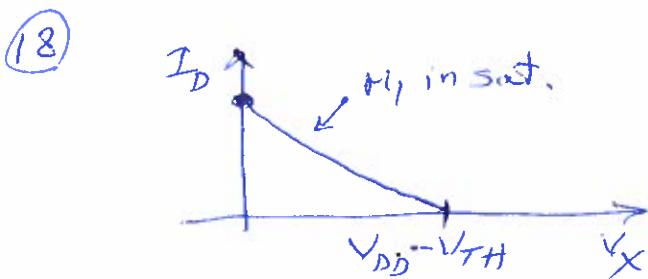⑰ Both are right. When using $g_m = \frac{2I_D}{V_{GS}-V_{TH}}$, we assume that I_D is constant and, inevitably, W/L is variable. For $g_m = \mu_n C_o x \frac{W}{L} (V_{GS}-V_{TH})$, on the other hand, we assume W/L is constant and I_D is variable.



⑲ If $|V_{DD} - |V_{TH}|| < V_i < V_{DD}$ $\Rightarrow M_1$ is off.

If V_i falls below $|V_{DD} - |V_{TH}||$, M_1 turns on in saturation.

As V_i falls to $|V_i - |V_{TH}||$, M_1 reaches the edge of triode region.

⑳

$$Rx = \frac{1}{gm} \quad Ry = \frac{1}{gm}$$

Due to the low resistance, these (diode-connected) devices cannot act as current sources.

㉑ General procedure: (1) determine which terminal is the source (the one with a lower potential), (2) see if the device is on ($V_{GS} \geq V_{TH}$), and (3) find the region of operation (triode or sat.)





- (a) off (b) off (c) triode (d) sat.

㉒ (a) off (b) sat. (c) triode (d) triode (e) triode (f) off
(g) sat. (h) sat. (i) sat.





㉓ (a) off (b) off (c) sat. (d) off

㉔ (a) sat. (b) triode (c) edge of triode (d) triode

(25)

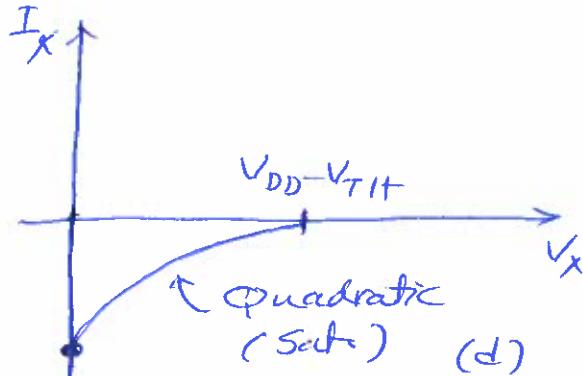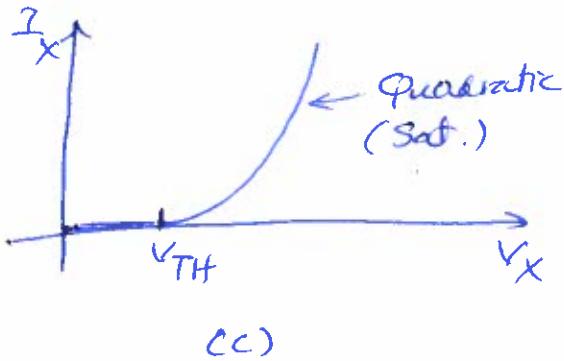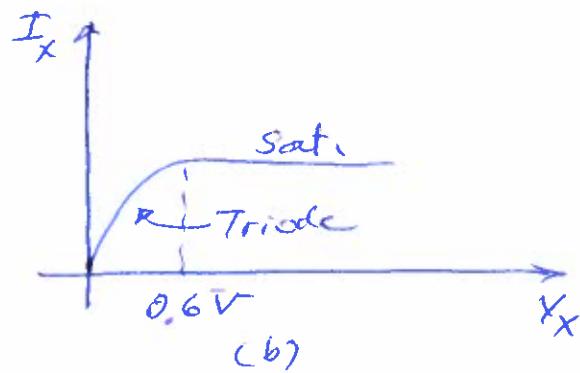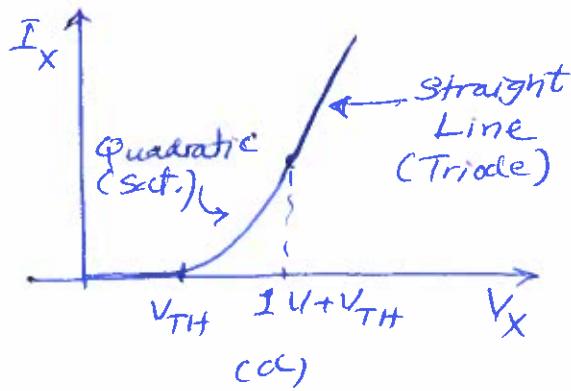

(26)

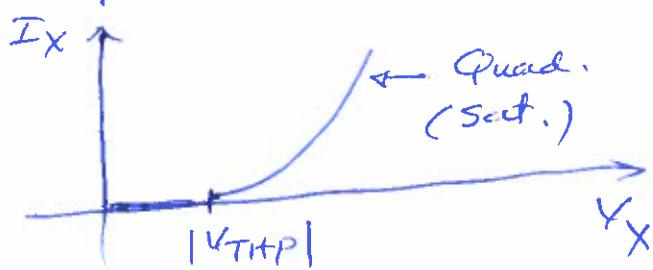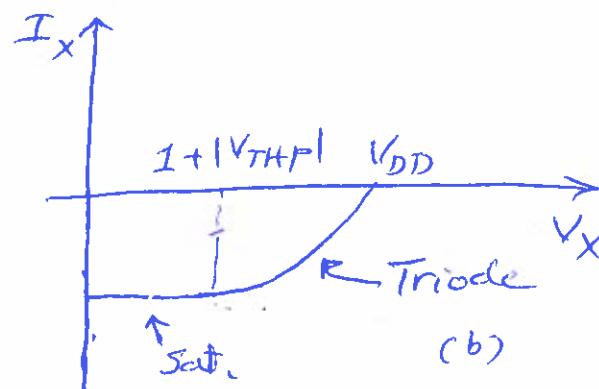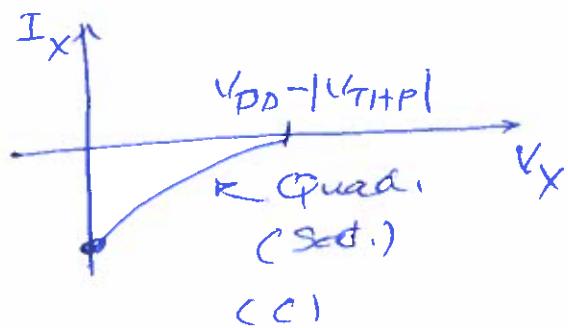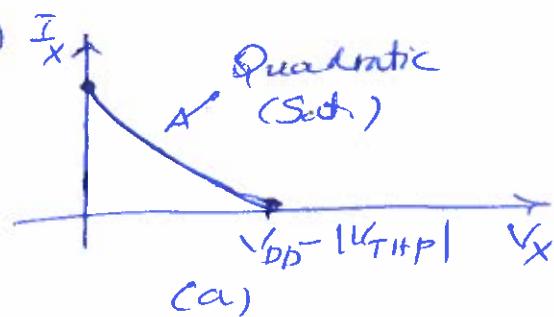

(27)



(28)

The two on the right cannot act as a current source because they exhibit a low output resistance ($\approx \frac{1}{g_m}$).

(29) In a CS stage, the input is applied to the gate and the output is sensed at the drain.

(30) $A_v = -g_m r_o$ if the current source is ideal.

(31) $A_v = -g_m, (r_{o1} \parallel r_{o2})$

(32) $A_v = \frac{-R_D}{\frac{1}{g_m} + R_S}$

(33) $A_v = \frac{-R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$

(34) $R_{out} = (1 + g_m r_o) R_S + r_o$

(35) $R_{out} = (1 + g_{m1} r_{o1}) r_{o2} + r_{o1}$

(36) In a CG stage, the input is applied to the source and the output is sensed at the drain.

(37) $R_{in} = \frac{1}{g_m}, R_{out} = R_D$

(38) $A_v = -g_{m1} (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m3}} \parallel r_{o3})$

(39) If $\lambda = 0$ for all transistors, $A_v \rightarrow \infty$.

If $r_{o2} < \infty$, $A_v = \frac{-r_{o2}}{\frac{1}{g_{m1}} + \frac{1}{g_{m3}}}$

(40) $\frac{V_{out2}}{V_{in}} = \frac{-\frac{1}{g_{m3}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} \quad \frac{V_{out1}}{V_{in}} = \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$